

بنام خدا



## طراحی سیستم‌های دیجیتال

نیم سال دوم ۱۴۰۲-۱۴۰۱

سوم

تمرین

۳۱ اردیبهشت ۱۴۰۲

موعد تحویل

- جواب سوالات را در قالب فایل PDF، به آدرس "khu.dsd98@gmail.com" با عنوان "A\_G\_3: stdName 1, stdName 2" ارسال کنید.
- تمرین ها را می توانید در گروه های دو نفره ارسال کنید که stdName 1 , stdName 2 نام اعضای گروه است.
- **مهم:** فایل PDF باید شامل کدهای VHDL قابل سنتز و اسکرین شات های RTL, post-mapping و compilation report فایل Test Bench و اسکرین شات Wave Form از Modelsim باشد.
- برای تکلیف ارسال شده با تاخیر نمره ای منظور نخواهد شد.
- تمامی Test Bench های شبیه سازی باید توسط Modelsим صورت پذیرد.

1. Let's assume that you are asked to implement a FIFO buffer for a 32-bit system. Write a synthesizable VHDL code describing the FIFO buffer, which includes FIFO controller and register file, for a 4-word FIFO (A FIFO containing 4 slots, each slot is 4 bytes). The FIFO buffer must have 2 components, one register file and one control unit!
  - Then, write a proper Testbench for this FIFO buffer and verify if the FIFO buffer works correctly or not. You need to examine underflow and overflow events in the simulation!

```

entity fifo_Buffer is
  port (clk, reset: in std_logic;
        wr, rd: in std_logic;
        w_data: in std_logic_vector (32-1 downto 0);
        full, empty: out std_logic;
        r_data: out std_logic_vector (32-1 downto 0)
  );
end fifo_Buffer;

```

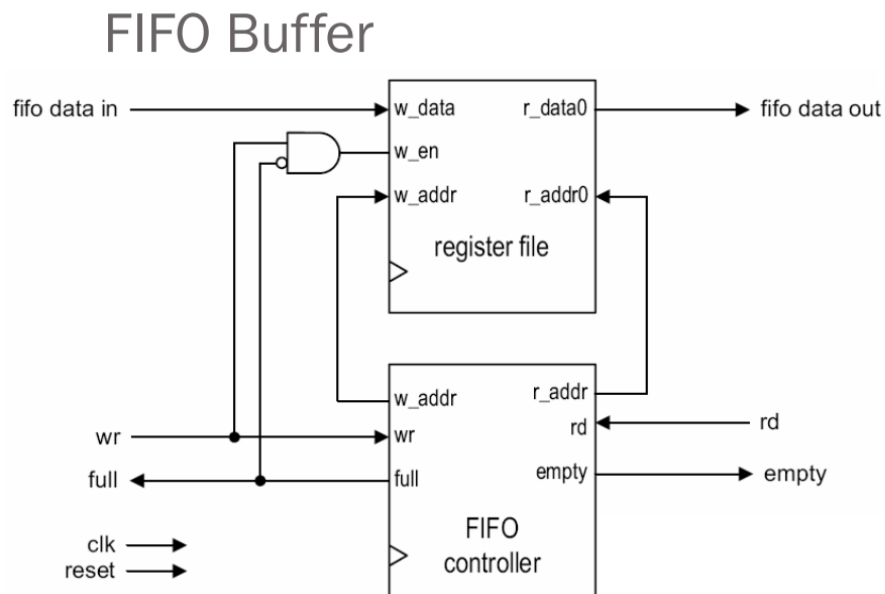


Figure 1: FIFO Buffer

2. Figure 2 shows an FSM which is used by a controller. This question asks you to:
  - 1- Draw its ASM Chart.
  - 2- Write a synthesizable VHDL code that implements the FSM.

3- The Moore output must be Glitch-free. To do so, you need to have a look-ahead output buffer.

 


Figure 2: An FSM

3. You need to design a fully qualified test bench to verify the 16-word CAM memory (fully-associative cache), which includes CAM controller and register file, to be used for a 4GB memory. This CAM memory is going to be used in a 64-bit CPU!

entity CAM\_Mem is

```

port ( clk, reset: in std_logic;
        wr_en      :in std_logic;
        key_in: in std_logic_vector (32-1 downto 0);
        data_in: in std_logic_vector (64-1 downto 0);
        hit: out std_logic;
        data_out: out std_logic_vector (64-1 downto 0)
    );

```

end CAM\_Mem;

